

CMSC 313
COMPUTER ORGANIZATION
&
ASSEMBLY LANGUAGE
PROGRAMMING

LECTURE ??, FALL 2012

TOPICS TODAY

- **Example: Sequence Detector**
- **Finite State Machine Simplification**
 - Circuit Minimization
 - State Reduction
 - State Assignment
 - Choice of Flip Flop

**EXAMPLE:
SEQUENCE DETECTOR**




Example: A Sequence Detector

 - **Example:** Design a machine that outputs a 1 when exactly two of the last three inputs are 1.
- *e.g.* input sequence of 011011100 produces an output sequence of 001111010.
- Assume input is a 1-bit serial line.
- Use D flip-flops and 8-to-1 Multiplexers.
- Start by constructing a state transition diagram (next slide).

Sequence Detector State Transition Diagram

- Design a machine that outputs a 1 when exactly two of the last three inputs are 1.



Sequence Detector State Table

Present state \ Input	<i>X</i>	
	0	1
<i>A</i>	<i>B/0</i>	<i>C/0</i>
<i>B</i>	<i>D/0</i>	<i>E/0</i>
<i>C</i>	<i>F/0</i>	<i>G/0</i>
<i>D</i>	<i>D/0</i>	<i>E/0</i>
<i>E</i>	<i>F/0</i>	<i>G/1</i>
<i>F</i>	<i>D/0</i>	<i>E/1</i>
<i>G</i>	<i>F/1</i>	<i>G/0</i>

Sequence Detector State Assignment

		Input	
		X	
Present state		0	1
	$s_2s_1s_0$	$s_2s_1s_0z$	$s_2s_1s_0z$
A:	000	001/0	010/0
B:	001	011/0	100/0
C:	010	101/0	110/0
D:	011	011/0	100/0
E:	100	101/0	110/1
F:	101	011/0	100/1
G:	110	101/1	110/0

(a)


Input and state at time t Next state and output at time $t+1$

s_2	s_1	s_0	x	s_2	s_1	s_0	z
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	0
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	0
0	1	0	1	1	1	0	0
0	1	1	0	0	1	1	0
0	1	1	1	1	0	0	0
1	0	0	0	1	0	1	0
1	0	0	1	1	1	0	1
1	0	1	0	0	1	1	0
1	0	1	1	1	0	0	1
1	1	0	0	1	0	1	1
1	1	0	1	1	1	0	0
1	1	1	0	d	d	d	d
1	1	1	1	d	d	d	d

(b)

Sequence Dectector

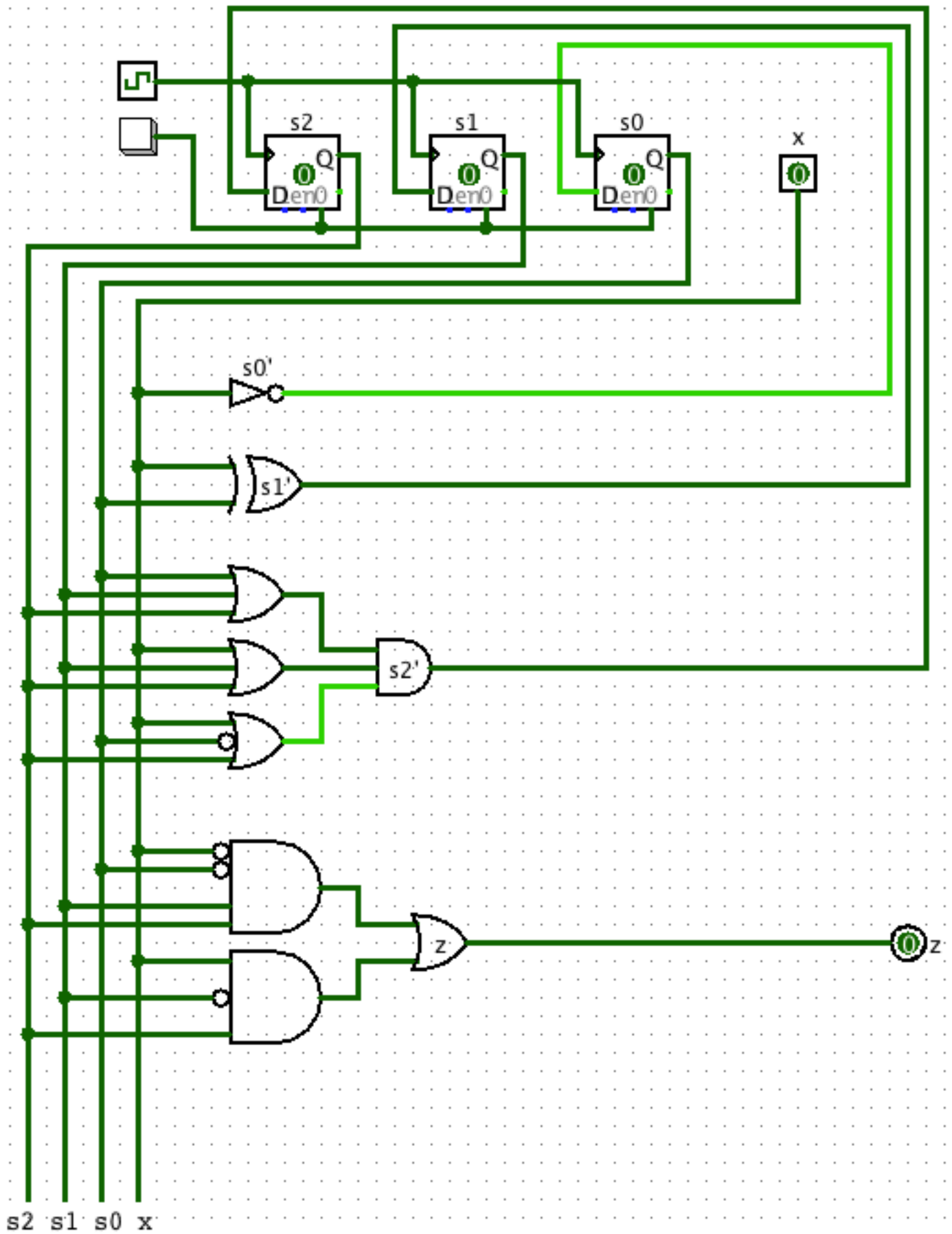Output 1 when EXACTLY two of last three bits are 1



FINITE STATE MACHINE SIMPLIFICATION




CIRCUIT MINIMIZATION



Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s1' = \overline{s0} x + s0 \overline{x} = s0 \text{ xor } x$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s0' = \overline{x}$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

Sequence Dectector (optimized)

 Output 1 when EXACTLY two of last three bits are 1



Notes on K-maps

- Also works for POS
- Takes 2^n time for formulas with n variables
- Only optimizes two-level logic
 - ◇ Reduces number of terms, then number of literals in each term
- Assumes inverters are free
- Does not consider minimizations across functions
- Circuit minimization is generally a hard problem
- Quine-McCluskey can be used with more variables
- CAD tools are available if you are serious

Karnaugh Maps

- ◇ **Implicant:** rectangle with 1, 2, 4, 8, 16 ... 1's
- ◇ **Prime Implicant:** an implicant that cannot be extended into a larger implicant
- ◇ **Essential Prime Implicant:** the only prime implicant that covers some 1
- ◇ **K-map Algorithm (not from M&H):**
 1. Find ALL the prime implicants. Be sure to check every 1 and to use don't cares.
 2. Include all essential prime implicants.
 3. Try all possibilities to find the minimum cover for the remaining 1's.

Circuit Minimization is Hard

- **Unix systems store passwords in encrypted form.**
 - ◇ User types in x , system computes $f(x)$ and looks for $f(x)$ in a file.
- **Suppose we use 64-bit passwords and I want to find the password x , such that $f(x) = y$. Let**
$$g_i(x) = 0 \text{ if } f(x) = y \text{ and the } i\text{th bit of } x \text{ is } 0$$
$$1 \text{ otherwise.}$$
- **If the i th bit of x is 1, then $g_i(x)$ outputs 1 for every x and has a very, very simple circuit.**
- **If you can simplify every circuit quickly, then you can crack passwords quickly.**

Simplifying Finite State Machines

- **State Reduction: equivalent FSM with fewer states**
- **State Assignment: choose an assignment of bit patterns to states (e.g., A is 010) that results in a smaller circuit**
- **Choice of flip-flops: use D flip-flops, J-K flip-flops or a T flip-flops? a good choice could lead to simpler circuits.**

STATE REDUCTION




State Reduction

- Description of state machine M_0 to be reduced.

Present state \ Input	X	
	0	1
A	$C/0$	$E/1$
B	$D/0$	$E/1$
C	$C/1$	$B/0$
D	$C/1$	$A/0$
E	$A/0$	$C/1$

 State Reduction Example: original transition diagram



State Reduction Algorithm


1. Use a 2-dimensional table — an entry for each pair of states.
2. Two states are "distinguished" if:
 - a. States X and Y of a finite state machine M are distinguished if there exists an input r such that the output of M in state X reading input r is different from the output of M in state Y reading input r .
 - b. States X and Y of a finite state machine are distinguished if there exists an input r such that M in state X reading input r goes to state X' , M in state Y reading input r goes to state Y' and we already know that X' and Y' are distinguished states.
3. For each pair (X, Y) , check if X and Y are distinguished using the definition above.
4. At the end of the algorithm, states that are not found to be distinguished are in fact equivalent.

State Reduction Table

- An **x** entry indicates that the pair of states are known to be distinguished.
- **A & B are equivalent, C & D are equivalent**

	A	B	C	D	E
A			x	x	x
B			x	x	x
C					x
D					x
E					

 State Reduction Example: reduced transition diagram



State Reduction Algorithm Performance

- As stated, the algorithm takes $O(n^4)$ time for a FSM with n states, because each pass takes $O(n^2)$ time and we make at most $O(n^2)$ passes.
- A more clever implementation takes $O(n^2)$ time.
- The algorithm produces a FSM with the fewest number states possible.
- Performance and correctness can be proven.

STATE ASSIGNMENT



The State Assignment Problem

- Two state assignments for machine M_2 .

Input \ P.S.	X	
	0	1
A	B/1	A/1
B	C/0	D/1
C	C/0	D/0
D	B/1	A/0

Machine M_2

Input \ S_0S_1	X	
	0	1
A: 00	01/1	00/1
B: 01	10/0	11/1
C: 10	10/0	11/0
D: 11	01/1	00/0

State assignment SA_0

Input \ S_0S_1	X	
	0	1
A: 00	01/1	00/1
B: 01	11/0	10/1
C: 11	11/0	10/0
D: 10	01/1	00/0

State assignment SA_1

State Assignment SA₀

- Boolean equations for machine M_2 using state assignment SA₀.

		X	
		0	1
S_0S_1	00		
	01	1	1
	11		
	10	1	1

$$S_0 = \bar{S}_0S_1 + S_0\bar{S}_1$$

		X	
		0	1
S_0S_1	00	1	
	01		1
	11	1	
	10		1

$$S_1 = \bar{S}_0\bar{S}_1\bar{X} + \bar{S}_0S_1X + S_0S_1\bar{X} + S_0\bar{S}_1X$$

		X	
		0	1
S_0S_1	00	1	1
	01		1
	11	1	
	10		

$$Z = \bar{S}_0\bar{S}_1 + \bar{S}_0X + S_0S_1\bar{X}$$

State Assignment SA₁

- Boolean equations for machine M_2 using state assignment SA₁.

		X	
		0	1
S ₀ S ₁	00		
	01	1	1
	11	1	1
	10		

$$S_0 = S_1$$

		X	
		0	1
S ₀ S ₁	00	1	
	01	1	
	11	1	
	10	1	

$$S_1 = \bar{X}$$

		X	
		0	1
S ₀ S ₁	00	1	1
	01		1
	11		
	10	1	

$$Z = \bar{S}_1\bar{X} + \bar{S}_0X$$


State Assignment Heuristics

- **No known efficient alg. for best state assignment**
- **Some heuristics (rules of thumb):**
 - ◇ **The initial state should be simple to reset — all zeroes or all ones.**
 - ◇ **Minimize the number of state variables that change on each transition.**
 - ◇ **Maximize the number of state variables that don't change on each transition.**
 - ◇ **Exploit symmetries in the state diagram.**
 - ◇ **If there are unused states (when the number of states s is not a power of 2), choose the unused state variable combinations carefully. (Don't just use the first s combination of state variables.)**
 - ◇ **Decompose the set of state variables into bits or fields that have well-defined meaning with respect to the input or output behavior.**
 - ◇ **Consider using more than the minimum number of states to achieve the objectives above.**

**APPLY
STATE REDUCTION
& STATE ASSIGNMENT
TO SEQUENCE DETECTOR**



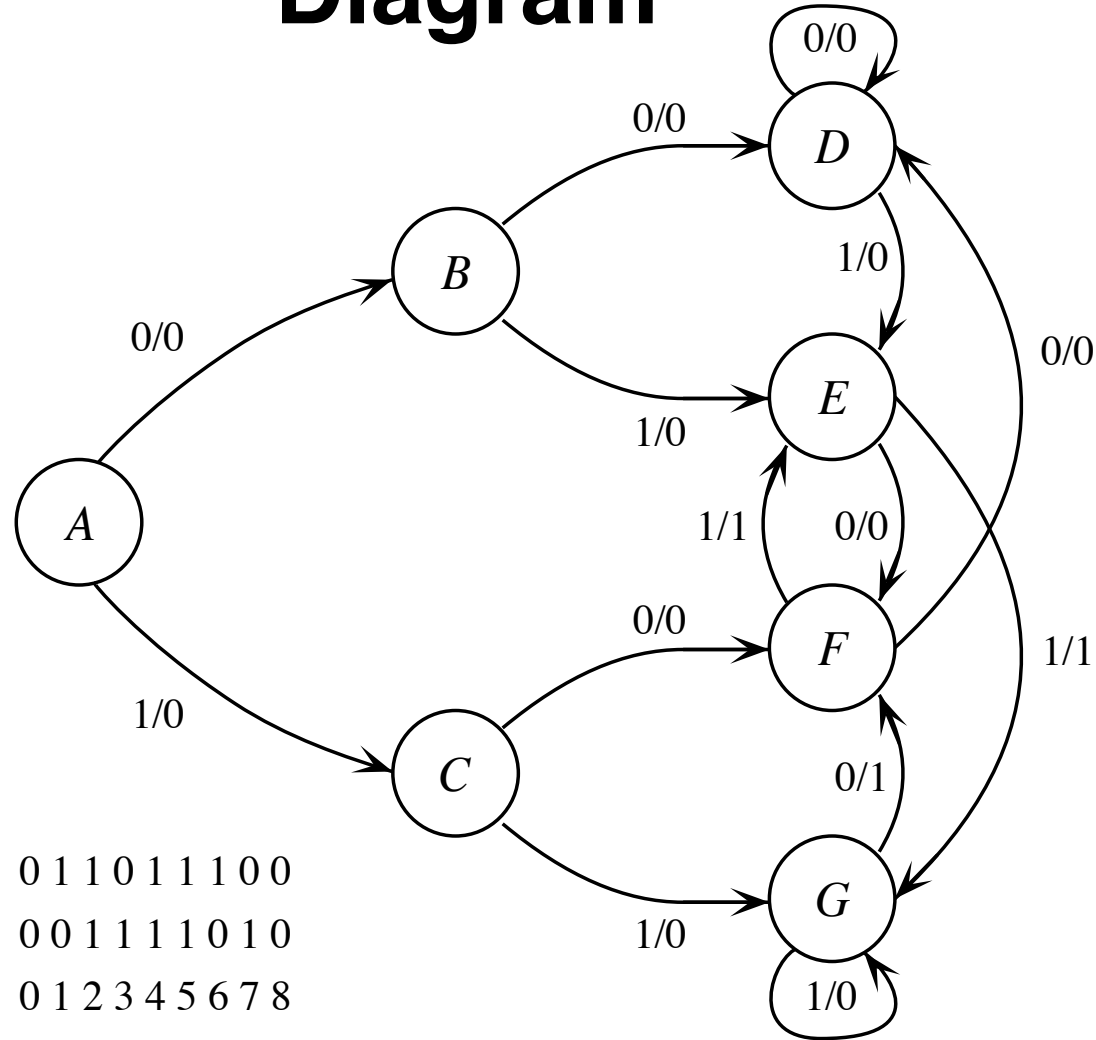Sequence Detector State Transition Diagram



Input: 0 1 1 0 1 1 1 0 0
 Output: 0 0 1 1 1 1 0 1 0
 Time: 0 1 2 3 4 5 6 7 8

Sequence Detector State Table

Present state \ Input	X	
	0	1
<i>A</i>	<i>B/0</i>	<i>C/0</i>
<i>B</i>	<i>D/0</i>	<i>E/0</i>
<i>C</i>	<i>F/0</i>	<i>G/0</i>
<i>D</i>	<i>D/0</i>	<i>E/0</i>
<i>E</i>	<i>F/0</i>	<i>G/1</i>
<i>F</i>	<i>D/0</i>	<i>E/1</i>
<i>G</i>	<i>F/1</i>	<i>G/0</i>


Sequence Detector State Reduction Table

	A	B	C	D	E	F	G
A	X	x	x	x	x	x	x
B	X	X	x		x	x	x
C	X	X	X	x	x	x	x
D	X	X	X	X	x	x	x
E	X	X	X	X	X	x	x
F	X	X	X	X	X	X	x
G	X	X	X	X	X	X	X

Sequence Detector Reduced State Table

Present state \ Input	X	
	0	1
A: A'	B'/0	C'/0
BD: B'	B'/0	D'/0
C: C'	E'/0	F'/0
E: D'	E'/0	F'/1
F: E'	B'/0	D'/1
G: F'	E'/1	F'/0

6-State Sequence Detector

 

Sequence Detector State Assignment

Present state \ Input	X	
	0	1
$S_2S_1S_0$	$S_2S_1S_0Z$	$S_2S_1S_0Z$
$A': 000$	001/0	010/0
$B': 001$	001/0	011/0
$C': 010$	100/0	101/0
$D': 011$	100/0	101/1
$E': 100$	001/0	011/1
$F': 101$	100/1	101/0

Sequence Detector K-Maps

- K-map reduction of next state and output functions for sequence detector.

	S_2S_1	00	01	11	10
S_0X	00	1		d	1
	01		1	d	1
	11	1	1	d	1
	10	1		d	

$$S_0 = \bar{S}_2\bar{S}_1\bar{X} + S_0X + S_2\bar{S}_0 + S_1X$$

	S_2S_1	00	01	11	10
S_0X	00			d	
	01	1		d	1
	11	1		d	
	10			d	

$$S_1 = \bar{S}_2\bar{S}_1X + S_2\bar{S}_0X$$

	S_2S_1	00	01	11	10
S_0X	00		1	d	
	01		1	d	
	11		1	d	1
	10		1	d	1

$$S_2 = S_2S_0 + S_1$$

	S_2S_1	00	01	11	10
S_0X	00			d	
	01			d	1
	11		1	d	
	10			d	1

$$Z = S_2\bar{S}_0X + S_1S_0X + S_2S_0\bar{X}$$

Improved Sequence Detector?

- **Formulas from the 7-state FSM:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x + s0 \overline{x} = s0 \text{ xor } x$$

$$s0' = \overline{x}$$

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

- **Formulas from the 6-state FSM:**

$$s2' = s2 s0 + s1$$

$$s1' = \overline{s2} \overline{s1} x + s2 \overline{s0} x$$

$$s0' = \overline{s2} \overline{s1} \overline{x} + s0 x + s2 \overline{s0} + s1 x$$

$$z = s2 \overline{s0} x + s1 s0 x + s2 s0 \overline{x}$$

Sequence Detector State Assignment

7-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

new 6-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	0	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	d	d	d	d
7	0	1	1	1	d	d	d	d
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	0	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

A = 000
 B = 001
 C = 010
 D = 011

E = 100
 F = 101
 G = 110

A = 000
 B/D = 001
 C = 010
~~D = 011~~

E = 100
 F = 101
 G = 110

6-State Sequence Detector

7-state

s0 x		s2 s1		s2	
		00	01	11	10
00	0	0	1	1	1
01	4	0	1	1	1
11	3	1	1	d	1
10	2	0	0	d	0

s1

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

new 6-state


s0 x		s2 s1		s2	
		00	01	11	10
00	0	0	1	1	1
01	4	0	1	1	1
11	3	1	d	d	1
10	2	0	d	d	0

s1

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$


6-State Sequence Detector

7-state

 

$$s1' = \overline{s0} x + s0 \overline{x}$$


new 6-state

 

$$s1' = \overline{s0} x$$


6-State Sequence Detector

7-state

 

$$s_0' = \bar{x}$$


new 6-state

 

$$s_0' = \bar{x}$$


6-State Sequence Detector

7-state

 

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

new 6-state

 

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

Improved Sequence Detector

- **Textbook formulas for the 6-state FSM:**

$$s2' = s2 s0 + s1$$

$$s1' = \overline{s2} \overline{s1} x + s2 \overline{s0} x$$

$$s0' = \overline{s2} \overline{s1} \overline{x} + s0 x + s2 \overline{s0} + s1 x$$

$$z = s2 \overline{s0} x + s1 s0 x + s2 s0 \overline{x}$$

- **New formulas for the 6-state FSM:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x$$

$$s0' = \overline{x}$$

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

CHOICE OF FLIP FLOP



Excitation Tables

- Each table shows the settings that must be applied at the inputs at time t in order to change the outputs at time $t+1$.

*S-R
flip-flop*

Q_t	Q_{t+1}	S	R
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

*D
flip-flop*

Q_t	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1



*J-K
flip-flop*

Q_t	Q_{t+1}	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

*T
flip-flop*

Q_t	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Serial Adder

  

- **State transition diagram, state table, and state assignment for a serial adder.**

	Input	XY			
Present state		00	01	10	11
A		A/0	A/1	A/1	B/0
B		A/1	B/0	B/0	B/1

Next state Output

	Input	XY			
Present state (S _p)		00	01	10	11
A:0		0/0	0/1	0/1	1/0
B:1		0/1	1/0	1/0	1/1

Serial Adder Next-State Functions

- Truth table showing next-state functions for a serial adder for D, S-R, T, and J-K flip-flops. Shaded functions are used in the example.


Present State			(Set) (Reset)						
X	Y	S_t	D	S	R	T	J	K	Z
0	0	0	0	0	0	0	0	d	0
0	0	1	0	0	1	1	d	1	1
0	1	0	0	0	0	0	0	d	1
0	1	1	1	0	0	0	d	0	0
1	0	0	0	0	0	0	0	d	1
1	0	1	1	0	0	0	d	0	0
1	1	0	1	1	0	1	1	d	0
1	1	1	1	0	0	0	d	0	1

J-K Flip-Flop Serial Adder Circuit


$$J = XY$$

$$K = \bar{X}\bar{Y}$$
 
$$Z = \bar{X}\bar{Y}S + \bar{X}Y\bar{S} + XY\bar{S} + X\bar{Y}S$$




D Flip-Flop Serial Adder Circuit

 

**CONSIDER
FLIP FLOP CHOICE
IN SEQUENCE DETECTOR**



6-State Sequence Detector

 

Sequence Detector State Assignment

7-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

new 6-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	0	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	d	d	d	d
7	0	1	1	1	d	d	d	d
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	0	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

A = 000
 B = 001
 C = 010
 D = 011

E = 100
 F = 101
 G = 110

A = 000
 B/D = 001
 C = 010
~~D = 011~~

E = 100
 F = 101
 G = 110

6-State Sequence Detector

	s2	s1	s0	x	s2'	s1'	s0'	z	j2	k2	j1	k1	j0	k0
0	0	0	0	0	0	0	1	0	0	<i>d</i>	0	<i>d</i>	1	<i>d</i>
1	0	0	0	1	0	1	0	0	0	<i>d</i>	1	<i>d</i>	0	<i>d</i>
2	0	0	1	0	0	0	1	0	0	<i>d</i>	0	<i>d</i>	<i>d</i>	0
3	0	0	1	1	1	0	0	0	1	<i>d</i>	0	<i>d</i>	<i>d</i>	1
4	0	1	0	0	1	0	1	0	1	<i>d</i>	<i>d</i>	1	1	<i>d</i>
5	0	1	0	1	1	1	0	0	1	<i>d</i>	<i>d</i>	0	0	<i>d</i>
6	0	1	1	0	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
7	0	1	1	1	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
8	1	0	0	0	1	0	1	0	<i>d</i>	0	0	<i>d</i>	1	<i>d</i>
9	1	0	0	1	1	1	0	1	<i>d</i>	0	1	<i>d</i>	0	<i>d</i>
10	1	0	1	0	0	0	1	0	<i>d</i>	1	0	<i>d</i>	<i>d</i>	0
11	1	0	1	1	1	0	0	1	<i>d</i>	0	0	<i>d</i>	<i>d</i>	1
12	1	1	0	0	1	0	1	1	<i>d</i>	0	<i>d</i>	1	1	<i>d</i>
13	1	1	0	1	1	1	0	0	<i>d</i>	0	<i>d</i>	0	0	<i>d</i>
14	1	1	1	0	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
15	1	1	1	1	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>

Q	Q'	J	K
0	0	0	<i>d</i>
0	1	1	<i>d</i>
1	0	<i>d</i>	1
1	1	<i>d</i>	0

6-State Sequence Detector

J2

		s2 s1		s2	
		00	01	11	10
s0 x	00	0 0	4 1	12 d	8 d
	01	1 0	5 1	13 d	9 d
s0	11	3 1	7 d	15 d	11 d
	10	2 0	6 d	14 d	10 d

s1

K2

		s2 s1		s2	
		00	01	11	10
s0 x	00	0 d	4 d	12 0	8 0
	01	1 d	5 d	13 0	9 0
s0	11	3 d	7 d	15 d	11 0
	10	2 d	6 d	14 d	10 1

s1

$$J2 = s1 + s0 x$$

$$K2 = s0 \bar{x}$$

6-State Sequence Detector

J1

s0 x		s2 s1		s2	
		00	01	11	10
0	00	0	d	d	0
1	01	1	d	d	1
3	11	0	d	d	0
2	10	0	d	d	0

s1

x

$$J1 = \overline{s0} x$$

K1

s0 x		s2 s1		s2	
		00	01	11	10
0	00	d	1	1	d
1	01	d	0	0	d
3	11	d	d	d	d
2	10	d	d	d	d

s1

x

$$K1 = \overline{x}$$

6-State Sequence Detector

J0

		s2 s1				s2	
	s0 x	00	01	11	10		
	00	0	4	12	8		
	01	1	5	13	9		
	11	3	7	15	11		
	10	2	6	14	10		
		s1					
						x	

The truth table for J0 shows the output for each combination of state bits s0 and s1. The output is 1 for (s0, s1) pairs (00, 00), (00, 01), (00, 11), and (00, 10). The output is 0 for (s0, s1) pairs (01, 00), (01, 01), (01, 11), and (01, 10). The output is 'd' (don't care) for all other combinations. A green rounded rectangle highlights the 01 row, and a vertical bracket labeled 'x' indicates that the output is independent of s2 for this row.

$$J0 = \overline{x}$$

K0

		s2 s1				s2	
	s0 x	00	01	11	10		
	00	0	4	12	8		
	01	1	5	13	9		
	11	3	7	15	11		
	10	2	6	14	10		
		s1					
						x	

The truth table for K0 shows the output for each combination of state bits s0 and s1. The output is 'd' for (s0, s1) pairs (00, 00), (00, 01), (00, 11), and (00, 10). The output is 1 for (s0, s1) pairs (11, 00) and (11, 10). The output is 0 for (s0, s1) pairs (10, 00) and (10, 10). The output is 'd' for all other combinations. A red rounded rectangle highlights the 01 row, and a vertical bracket labeled 'x' indicates that the output is independent of s2 for this row.

$$K0 = x$$

Improved Sequence Detector

- **Formulas for the 6-state FSM with D Flip-flops:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x$$

$$s0' = \overline{x}$$

- **Formulas for the 6-state FSM with J-K Flip-flops:**

$$J2 = s1 + s0 x \quad K2 = s0 \overline{x}$$

$$J1 = \overline{s0} x \quad K1 = \overline{x}$$

$$J0 = \overline{x} \quad K0 = x$$

Sequence Dectector (J-K flip flops)

Output 1 when EXACTLY two of last three bits are 1

