



## CMPE 413 Lab

(4) Include waveforms that show the flip-flop failing to latch the correct data for both cases (from the parametric sweeps). There should be waveforms for the coarse grained sweep as well as the fine grained sweep.

(5) Generate the following plots and determine the times values given below for both cases. Report all the data in a table.

- Plot the clk-to-q ( $t_{cq}$ ) delay (y-axis) versus the d-to-clk ( $t_{dc}$ ) delay (x-axis). Determine the following time values:
  1. Min Delay: minimum  $t_{cq}$  value (i.e.  $t_{cq}$  when d changes a “long time” before clk)
  2. Failing Delay:  $t_{dc}$  when the flip-flop fails to latch the correct value
  3. Setup Time 1:  $t_{dc}$  when the  $t_{cq}$  increases by 10% over the minimum value
- Plot the total d-to-q ( $t_{dq}$ ) delay (y-axis) versus the d-to-clk ( $t_{dc}$ ) delay (x-axis). Determine the following time value:
  1. Setup Time 2:  $t_{dc}$  when the  $t_{dq}$  is minimum
- You need to generate the plots and determine the time values for both cases i.e. the flip-flop latching a 1 as well as latching a 0.

(6) Use the guidelines outlined in Lab 2 for the report. All the plots should be labelled, captioned and referred to in your write-up. The write-up should be brief and contain the simulation parameters used for each experiment and describe the corresponding plots.

(7) Submit a single pdf file for your report using submit, the class name is cmpe315\_cpatel2 and the project name is lab4.

**THE LABS ARE INDIVIDUAL EFFORTS: INSTANCES OF CHEATING WILL RESULT IN YOU FAILING THE COURSE.**