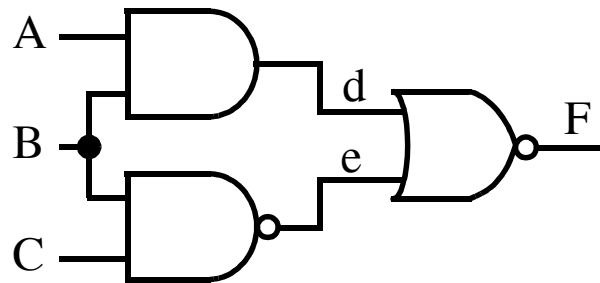


D-Algorithm -- Roth (IBM 1966)

Roth's D-Algorithm (D-ALG) defined the calculus and algorithms for ATPG using D-cubes.

Definitions

- ◆ *Singular cover*: Defined to be the minimal set of input signal assignments needed to represent *essential prime implicants* in Karnaugh map.



<i>AND</i>	<i>a</i>	<i>b</i>	<i>d</i>	<i>NOR</i>	<i>d</i>	<i>e</i>	<i>F</i>
1	0	X	0	4	1	X	0
2	X	0	0	5	X	1	0
3	1	1	1	6	0	0	1

D-Calculus and D-Algorithm

- ◆ *D-cube*: A collapsed truth table entry.

For example, combine rows 3 and 1 of the AND gate singular cover, and express it in Roth's 5-valued algebra (row 3 is good machine).

D 1 D

Rows 3 and 2 yield the *propagation D-cube*:

1 D D

A third is *D D D*

Inverting D to \bar{D} in each of these yields the 6 *D-cubes* for the AND gate.

3 of the NOR gate *D-cubes* are:

D 0 \bar{D}

0 D \bar{D}

D D \bar{D}

D-Calculus and D-Algorithm

- ◆ ***D-intersection***: Define how different ***D-cubes*** can coexist for different gates in a logic circuit.

$$0 \cap 0 = 0 \cap X = X \cap 0 = 0$$

$$1 \cap 1 = 1 \cap X = X \cap 1 = 1$$

$$X \cap X = X$$

Rule: If one cube assigns a specific signal value, the other cubes must assign either the same signal or X

For example, $0 X X$ intersect $1 X X$ is the empty cube (incompatible).

<i>D-intersection</i>	<i>0</i>	<i>1</i>	<i>X</i>	<i>D</i>	\overline{D}
0	0	ϕ	0	ψ	ψ
1	ϕ	1	1	ψ	ψ
X	0	1	X	D	\overline{D}
D	ψ	ψ	D	μ	λ
\overline{D}	ψ	ψ	\overline{D}	λ	μ

D-Calculus and D-Algorithm

◆ *D-intersection* (contd.):

The greek symbols ϕ and ψ represent incompatible assignments.

If the values are incompatible during propagation or implications, the assignment is called *inconsistent* and *backtracking* is necessary.

Greek symbols μ and λ indicate incompatibilities if *both* are present in *D-cubes* with multiple input D and \bar{D} .

For example, if only 1 occurs, invert the D s in the second cube and perform intersection.

◆ *D-contains*: A cube A *D-contains* cube B if the set of A cube vertices contains (is a superset of) the B cube vertices.

D-Calculus and D-Algorithm

◆ *Primitive D-cubes of failure (PDF)*: These model faults including:

- ❑ *SA0* (represented by D)
- ❑ *SA1* (represented by \bar{D})
- ❑ Bridging faults (short circuits)
- ❑ Arbitrary change in logic gate function (e.g., from AND to OR).

For the AND gate, the *PDF* for output *SA0* is $1\ 1\ D$

Here the good machine generates a 1 when both inputs are 1 , while the bad machine generates a 0 .

The *PDF*s for the AND gate output *SA1* are $0\ X\ \bar{D}$ and $X\ 0\ \bar{D}$.

Note the *PDF* are distinct from the *propagation D-cubes*.

The former models a failure at the gate.

The latter models the conditions for fault effect propagation.


D-Calculus and D-Algorithm

◆ *Implication procedure*: Consists of the following steps:


- ❑ Model the fault with the appropriate *PDF*.
- ❑ Select *propagation D-cubes* to propagate fault-effect to PO(s) (*D-drive procedure*).
- ❑ Select singular cover cubes to justify internal circuit signals (*consistency procedure*).

The D-algorithm's main problem is that it selects cubes and singular covers arbitrarily during test generation.

D-ALG

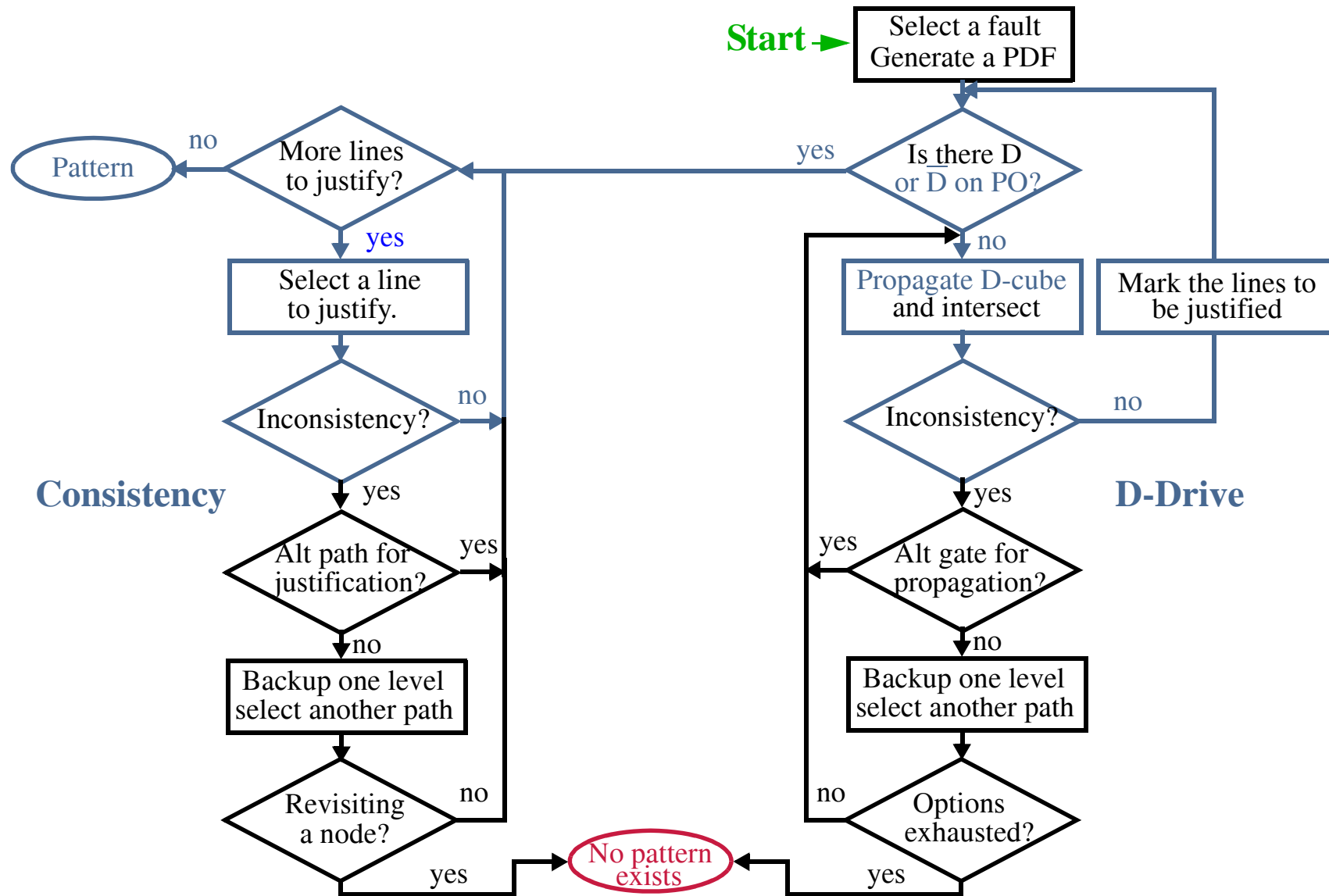

D-ALG Examples

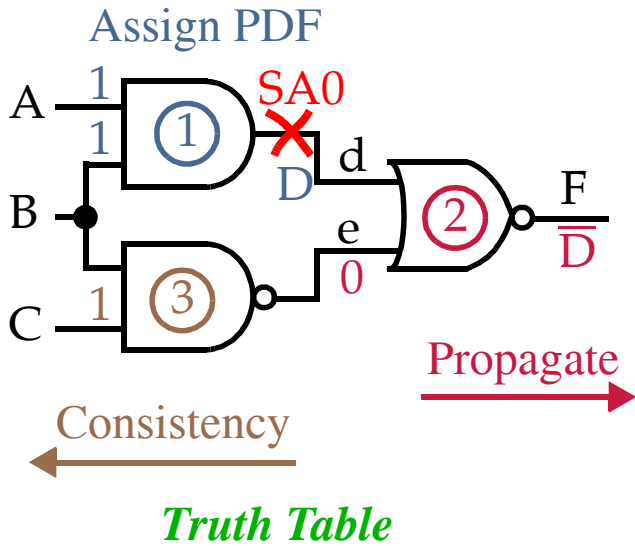

Singular Cover

<i>A</i>	<i>B</i>	<i>C</i>	<i>d</i>	<i>e</i>	<i>F</i>
1	1		1		
0			0		
	0		0		
	1	1		0	
	0			1	
		0		1	
				1	0
			1		0
			0	0	1

Truth Table

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Propagation D-cubes


<i>A</i>	<i>B</i>	<i>C</i>	<i>d</i>	<i>e</i>	<i>F</i>
D	1		D		
1	D		D		
D	D		D		
	D	1		\overline{D}	
	1	D		\overline{D}	
	D	D		\overline{D}	
			D	0	\overline{D}
			0	D	\overline{D}
			D	D	\overline{D}

D-ALG Examples

The following procedure is carried out for *d SA0* in the previous circuit:

Step	A	B	C	d	e	F	Type of cube
1	1	1		D			PDF for AND gate
2				D	0	\bar{D}	Propagation D-cube for NOR gate
3		1	1		0		Singular cover of NAND gate

Example #2:

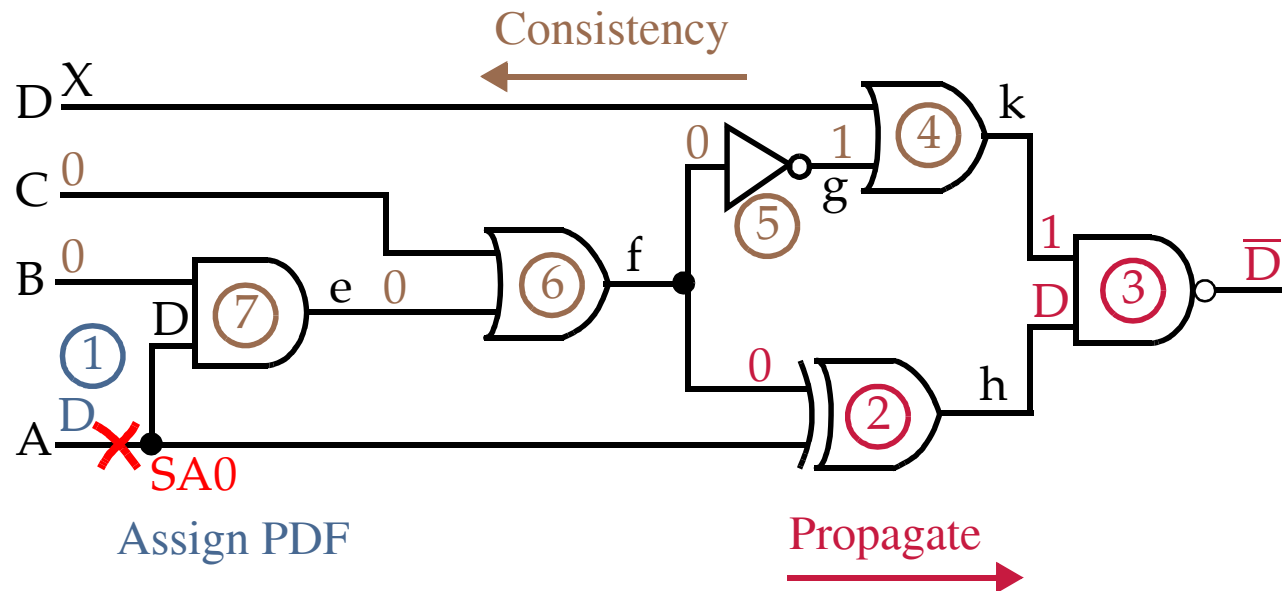

D-ALG Examples

Steps followed to generate *test cube (tc)*:

	<i>Step</i>		<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>e</i>	<i>f</i>	<i>g</i>	<i>h</i>	<i>k</i>	<i>L</i>
<i>D-drive</i>	1		D									
	2		D					0		D		
	3		D					0		D	1	\bar{D}
<i>Consistency</i>	4	or							1		1	
	5	not						0	1			
	6	or			0		0	0				
	7	and		0			0					
		tc	D	0	0		0	0	1	D	1	\bar{D}
<i>D-chain</i> dies												

This example and table is given in Roth's paper.


Several other examples are covered in the paper.

Note that all implications are performed in the *consistency* procedure here.

A later example by our authors indicates *the implications* are carried out after each *D propagation* step in the *D-drive*?


D-ALG Examples

Example #3

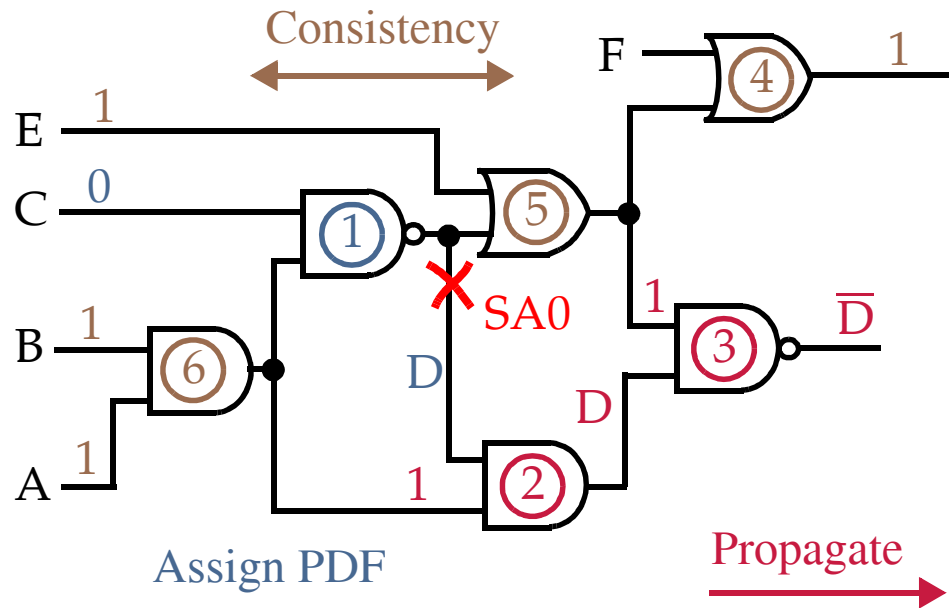

D-ALG Examples

Example #4

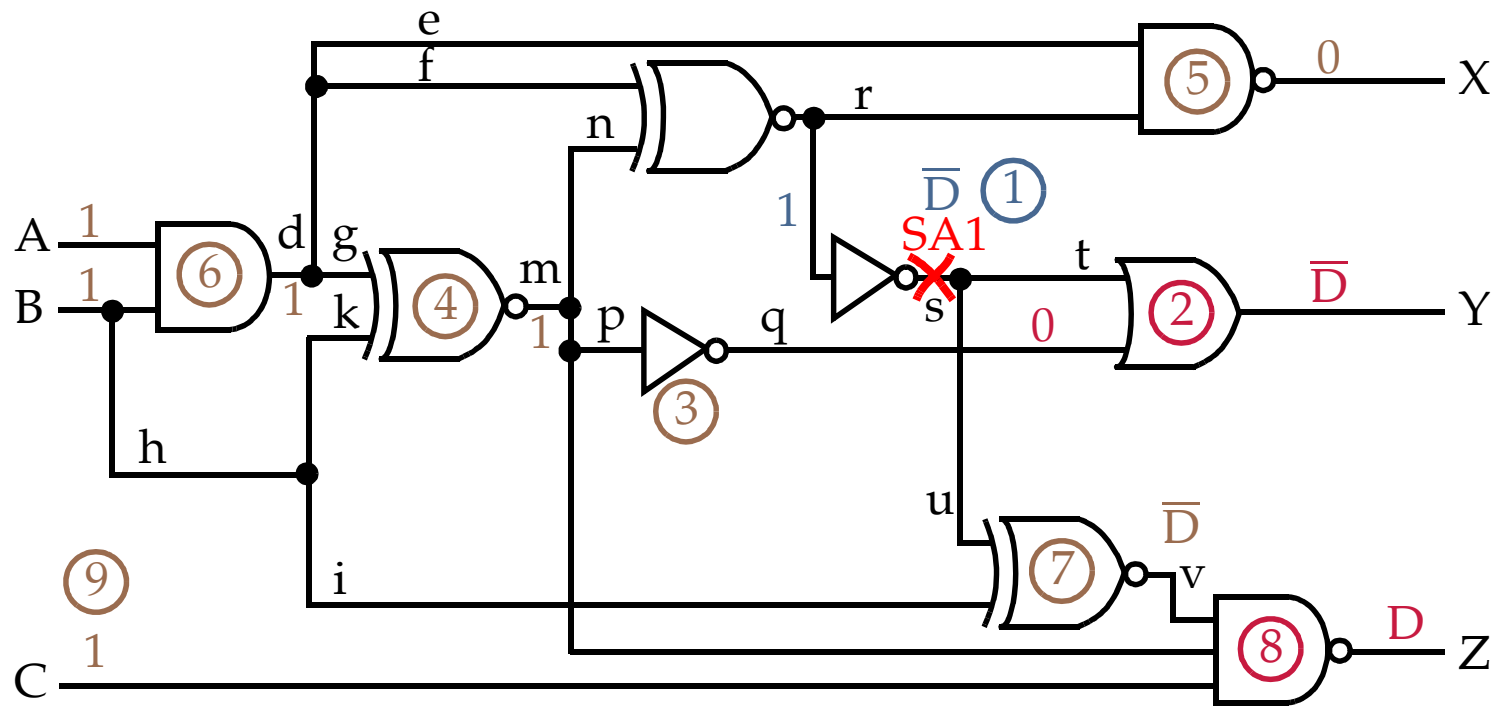

Assign PDF Propagate Consistency