

# Datapaths and Control

---

- Digital systems perform sequences of operations on encoded data
- *Datapath*
  - Combinational circuits for operations
  - Registers for storing intermediate results
- *Control section*: control sequencing
  - Generates *control signals*
    - Selecting operations to perform
    - Enabling registers at the right times
  - Uses *status signals* from datapath

# Example: Complex Multiplier

- Cartesian form, fixed-point
  - operands: 4 integer, 12 fraction bits
  - result: 8 pre-, 24 post-binary-point bits


- Subject to tight area constraints

$$a = a_r + ja_i \qquad b = b_r + jb_i$$

$$p = ab = p_r + jp_i = (a_r b_r - a_i b_i) + j(a_r b_i + a_i b_r)$$

- 4 multiplies, 1 add, 1 subtract
  - Perform sequentially using 1 multiplier, 1 adder/subtracter

# Complex Multiplier Datapath

 

# Complex Multiplier in Verilog

```
module multiplier
  ( output reg signed [7:-24] p_r, p_i,
    input  signed [3:-12] a_r, a_i, b_r, b_i,
    input                                     clk, reset, input_rdy );
  reg a_sel, b_sel, pp1_ce, pp2_ce, sub, p_r_ce, p_i_ce;
  wire signed [3:-12] a_operand, b_operand;
  wire signed [7:-24] pp, sum
  reg signed [7:-24] pp1, pp2;
  ...
```

# Complex Multiplier in Verilog

```
assign a_operand = ~a_sel ? a_r : a_i;
assign b_operand = ~b_sel ? b_r : b_i;
assign pp = {{4{a_operand[3]}}, a_operand, 12'b0} *
           {{4{b_operand[3]}}, b_operand, 12'b0};
always @(posedge clk) // Partial product 1 register
  if (pp1_ce) pp1 <= pp;
always @(posedge clk) // Partial product 2 register
  if (pp2_ce) pp2 <= pp;
assign sum = ~sub ? pp1 + pp2 : pp1 - pp2;
always @(posedge clk) // Product real-part register
  if (p_r_ce) p_r <= sum;
always @(posedge clk) // Product imaginary-part register
  if (p_i_ce) p_i <= sum;
...
endmodule
```

# Multiplier Control Sequence

- Avoid resource conflict
- First attempt
  1.  $a_r * b_r \rightarrow pp1\_reg$
  2.  $a_i * b_i \rightarrow pp2\_reg$
  3.  $pp1 - pp2 \rightarrow p\_r\_reg$
  4.  $a_r * b_i \rightarrow pp1\_reg$
  5.  $a_i * b_r \rightarrow pp2\_reg$
  6.  $pp1 + pp2 \rightarrow p\_i\_reg$
- Takes 6 clock cycles

# Multiplier Control Sequence

- Merge steps where no resource conflict
- Revised attempt
  1.  $a_r * b_r \rightarrow pp1\_reg$
  2.  $a_i * b_i \rightarrow pp2\_reg$
  3.  $pp1 - pp2 \rightarrow p\_r\_reg$   
 $a_r * b_i \rightarrow pp1\_reg$
  4.  $a_i * b_r \rightarrow pp2\_reg$
  5.  $pp1 + pp2 \rightarrow p\_i\_reg$
- Takes 5 clock cycles

# Multiplier Control Signals

Step	a_sel	b_sel	pp1_ce	pp2_ce	sub	p_r_ce	p_i_ce
1	0	0	1	0	–	0	0
2	1	1	0	1	–	0	0
3	0	1	1	0	1	1	0
4	1	0	0	1	–	0	0
5	–	–	0	0	0	0	1




# Finite-State Machines

---

- Used to implement control sequencing
- A FSM is defined by
  - set of inputs
  - set of outputs
  - set of states
  - initial state
  - transition function
  - output function
- States are steps in a sequence of transitions
  - There are “Finite” number of states.

# FSM in Hardware

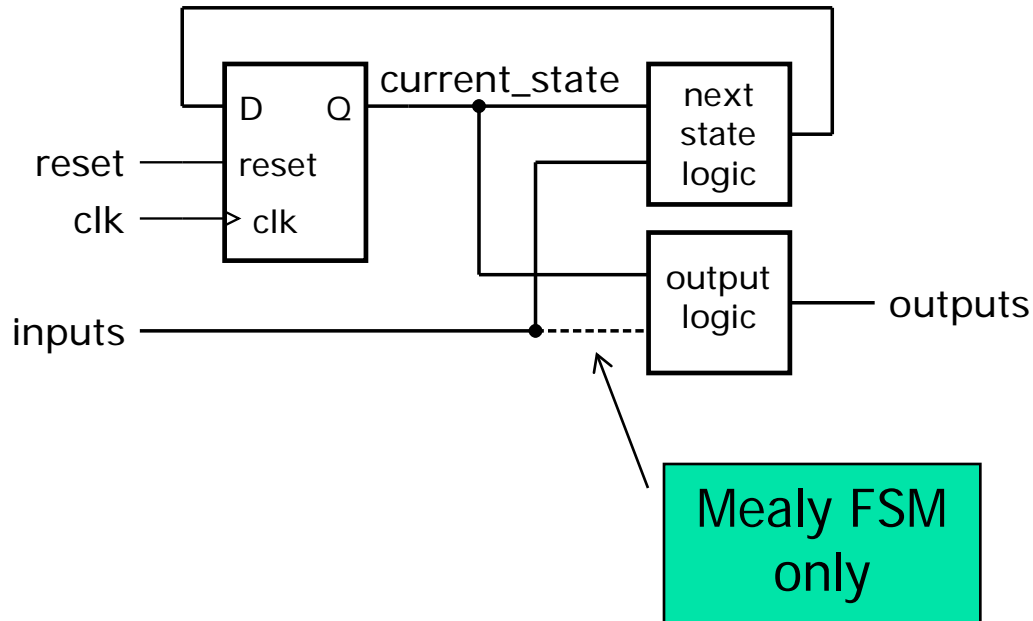

- Mealy FSM: outputs depend on state and inputs
- Moore FSM: outputs depend on state only (no dash)
- Mealy and Moore FSM can convert to each other

# FSM Example: Multiplier Control

- One state per step
- Separate idle state?
  - Wait for `input_rdy = 1`
  - Then proceed to steps 1, 2, ...
  - But this wastes a cycle!
- Use step 1 as idle state
  - Repeat step 1 if `input_rdy ≠ 1`
  - Proceed to step 2 otherwise
- Output function
  - Defined by table on slide 43
  - Moore or Mealy?

Transition function

current_ state	input_ rdy	next_ state
step1	0	step1
step1	1	step2
step2	–	step3
step3	–	step4
step4	–	step5
step5	–	step1

# State Encoding

- Encoded in binary
  - $N$  states: use at least  $\lceil \log_2 N \rceil$  bits
- Encoded value used in circuits for transition and output function
  - encoding affects circuit complexity
- Optimal encoding is hard to find
  - CAD tools can do this well
- One-hot works well in FPGAs
- Often use 000...0 for idle state
  - reset state register to idle

# FSMs in Verilog

- Use parameters for state values
  - Synthesis tool can choose an alternative encoding

```
parameter [2:0] step1 = 3' b000, step2 = 3' b001,  
                step3 = 3' b010, step4 = 3' b011,  
                step5 = 3' b100;  
reg [2:0] current_state, next_state ;  
...
```

# Multiplier Control in Verilog

```
always @(posedge clk or posedge reset) // State register
  if (reset) current_state <= step1;
  else      current_state <= next_state;
always @* // Next-state logic
  case (current_state)
    step1: if (!input_rdy) next_state = step1;
           else           next_state = step2;
    step2:           next_state = step3;
    step3:           next_state = step4;
    step4:           next_state = step5;
    step5:           next_state = step1;
  endcase
```

# Multiplier Control in Verilog


```
always @* begin // Output_logic
  a_sel = 1'b0; b_sel = 1'b0; pp1_ce = 1'b0; pp2_ce = 1'b0;
  sub = 1'b0; p_r_ce = 1'b0; p_i_ce = 1'b0;
  case (current_state)
    step1: begin
      pp1_ce = 1'b1;
    end
    step2: begin
      a_sel = 1'b1; b_sel = 1'b1; pp2_ce = 1'b1;
    end
    step3: begin
      b_sel = 1'b1; pp1_ce = 1'b1;
      sub = 1'b1; p_r_ce = 1'b1;
    end
    step4: begin
      a_sel = 1'b1; pp2_ce = 1'b1;
    end
    step5: begin
      p_i_ce = 1'b1;
    end
  endcase
end
```

# State Transition Diagrams

- Bubbles to represent states
- Arcs to represent transitions

 - Example

- $S = \{s1, s2, s3\}$
- Inputs  $(a1, a2)$ :  
 $\Sigma = \{(0,0), (0,1), (1,0), (1,1)\}$
- $\delta$  defined by diagram





# State Transition Diagrams

- Annotate diagram to define output function
  - Annotate states for Moore-style outputs
  - Annotate arcs for Mealy-style outputs
- Example
  - $x_1, x_2$ : Moore-style
  - $y_1, y_2, y_3$ : Mealy-style

